

Product Of Sums Boolean Algebra

Product Of Sums Boolean Algebra

Downloaded from [remodelicious.com](#) by Bridget & Riggs

UNDERSTANDING PRODUCT OF SUMS IN BOOLEAN ALGEBRA

Boolean algebra is the mathematical foundation of digital logic design, computer science, and electronic circuit optimization. Among its most powerful concepts are the **Product of Sums (POS)** forms. Whether you are a student learning logic gates, a designer working on FPGA programming, or a professional optimizing circuit performance, mastering the product of sums boolean algebra technique is essential. This article provides a comprehensive, natural exploration of the topic, walking through definitions, derivation methods, advantages, and practical applications.

What Is Product of Sums (POS) in Boolean Algebra?

In Boolean algebra, any logical expression can be represented in one of two standard forms: Sum of Products (SOP) or Product of Sums (POS). The **product of sums** form is a logical AND of multiple OR terms. Each OR term is called a "sum term" because the OR operation is analogous to addition in Boolean arithmetic. An example of a POS expression is:

$$(A + B) \cdot (C + \bar{D}) \cdot (\bar{A} + B + C)$$

Here, each sum term contains variables or their complements combined with the OR operator, and the entire expression is the AND (product) of these sum terms. POS expressions are particularly useful when implementing circuits using NOR logic or when simplifying expressions for specific hardware constraints.

The Dual Relationship with Sum of Products

To fully appreciate product of sums boolean algebra, we must understand its dual: the Sum of Products form. SOP expressions are ORs of AND terms (minterms). POS expressions are ANDs of OR terms (maxterms). This duality is a fundamental principle of Boolean algebra: every theorem has a dual obtained by swapping AND with OR and 0 with 1. For example, De Morgan's laws directly relate the two forms. Converting between SOP and POS is often necessary when optimizing a circuit for speed, power, or component availability.

Why Use Product of Sums?

Engineers and designers choose the POS form for several reasons:

- Implementation with NOR gates:** NOR gates are universal and often simpler to realize in certain logic families. A POS expression directly maps to a two-level NOR-NOR logic network.
- Fewer logic levels:** In some cases, the POS form results in fewer gate delays compared to the SOP equivalent.
- Reduced fan-in:** Depending on the expression, sum terms may have fewer variables, reducing gate input requirements.
- Easier handling of don't-care conditions:** When simplifying expressions with don't-care states, POS can sometimes produce a more compact representation.

Understanding these practical benefits helps you decide when to apply product of sums boolean algebra in real-world scenarios.

DERIVING THE PRODUCT OF SUMS FORM

There are several methods to obtain a POS expression from a given Boolean function. We will explore the three most common techniques: from the truth table using maxterms, algebraic manipulation, and using Karnaugh maps.

From Truth Table: The Maxterm Approach

The most systematic way to derive a POS expression is to list the rows of the truth table where the output is **0**. For each such row, we write a sum term (maxterm) that is false for that combination. Then we AND all these maxterms together. A maxterm is the OR of all variables, with each variable complemented if it is 1 in the row, and uncomplemented if it is 0. This ensures the sum term equals 0 only for that specific input combination. By ANDing all maxterms, the entire expression is 0 exactly when any one of those conditions holds, which corresponds to the desired output.

For example, consider a function F that is 0 for the rows (0,0), (1,0), and (1,1) of two variables A and B. The maxterms for these rows are:

- Row (0,0): $A + B$
- Row (1,0): $\bar{A} + B$

- Row (1,1): $\bar{A} + \bar{B}$

The POS expression becomes $(A + B) \cdot (\bar{A} + B) \cdot (\bar{A} + \bar{B})$. This expression implements the function F which is 1 only when (A=0, B=1).

Using Karnaugh Maps for POS Simplification

A Karnaugh map (K-map) is a visual tool to simplify Boolean expressions. While most people use K-maps to find minimal SOP forms, they are equally powerful for product of sums boolean algebra. Instead of grouping the 1s, we group the **0s** (complement of the function). Each group of 0s corresponds to a sum term. The procedure:

- Draw the K-map for the function and mark cells with 0 and 1.
- Identify adjacent cells containing 0s and form the largest possible rectangular groups (powers of two, wrapping edges).
- For each group (which represents a prime implicate), write the sum term that is 0 for all cells in the group. This is done by taking the variables that remain constant within the group: if a variable is 0 in all cells of the group, it appears uncomplemented in the sum term; if it is 1, it appears complemented; if it varies, it is omitted.
- AND all the sum terms together to obtain the minimal POS expression.

For example, a K-map with three variables where 0s occupy cells (0,0,0), (0,0,1), and (1,1,0) might simplify to $(A + B) \cdot (\bar{A} + B + \bar{C})$.

Algebraic Manipulation and De Morgan's Law

If you already have an SOP expression, you can algebraically transform it into POS by applying De Morgan's theorem and duality. The steps:

- Compute the complement (NOT) of the original function.
- Simplify the complement using SOP methods.
- Take the complement again using De Morgan's law, which converts the SOP into a POS form. This directly yields the product of sums representation.

For instance, consider $F = A \cdot B + \bar{A} \cdot C$. Its complement is $\bar{F} = (\bar{A} + \bar{B}) \cdot (A + \bar{C})$ after applying De Morgan and distribution. Then $F = (\bar{F}) = (A + B) \cdot (\bar{A} + C)$ — a POS expression. This method is useful when you already have an algebraic expression but need a POS form for implementation.

COMPARING POS AND SOP IN CIRCUIT DESIGN

When designing digital circuits, you must choose between product of sums boolean algebra and sum of products. Both yield two-level logic implementations, but the gate types differ. SOP uses AND-OR logic (NAND-NAND if using universal gates), while POS uses OR-AND logic (NOR-NOR).

Area and Speed Considerations

The minimal SOP and minimal POS forms are usually different, and which one is smaller depends on the function. Functions with many 1s tend to have simpler SOP, while functions with many 0s often yield simpler POS. However, the true minimal expression may be a mixture of both (multi-level logic). For programmable logic devices like PLAs and FPGAs, the choice can affect resource usage. Many synthesis tools automatically choose the best form, but understanding the underlying math helps you interpret results and resolve timing issues.

Don't-Care Conditions

Don't-care conditions (inputs that never occur or whose output we don't care about) can be exploited to simplify POS expressions. When grouping 0s in a K-map, you can treat don't-care cells as either 0 or 1 to form larger groups, reducing the number of literals and gates. This flexibility often leads to more efficient circuits.

EXAMPLES AND STEP-BY-STEP WALKTHROUGHS

Example 1: Three-Variable Function

Let $F(A, B, C) = \sum m(0, 2, 4, 6)$ (output 1 for minterms 0, 2, 4, 6). The truth table shows the function is 0 for rows 1,3,5,7. We write maxterms:

- Row 1 (001): $A + B + \bar{C}$
- Row 3 (011): $A + \bar{B} + \bar{C}$
- Row 5 (101): $\bar{A} + B + \bar{C}$
- Row 7 (111): $\bar{A} + \bar{B} + \bar{C}$

POS: $(A + B + \bar{C}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$. Notice that $\bar{C}$ appears in all sum terms, so we can factor: $(\bar{C}) \cdot (A + B) \cdot (A + \bar{B}) \cdot (\bar{A} + B) \cdot (\bar{A} + \bar{B})$. The last four terms simplify to $(A + B) \cdot (A + \bar{B}) = A$, and $(\bar{A} + B) \cdot (\bar{A} + \bar{B}) = \bar{A}$, so the entire POS reduces to $\bar{C}$. The function is simply NOT C. This demonstrates how POS simplification can reveal a trivial solution.

Example 2: A Practical Decoder

Consider a 2-to-4 decoder with enable. The output $Y0 = \text{enable} \cdot \bar{A} \cdot \bar{B}$. A typical POS implementation for one output might be derived from its 0s. The product of sums boolean algebra helps when outputs are active-low. For example, an active-low output can be directly implemented using NOR gates from the POS form.

COMMON PITFALLS AND MISCONCEPTIONS

- **Confusing sum and product:** Remember that "sum" means OR, "product" means AND. In POS, you are multiplying sum terms.
- **Ignoring the complement in maxterms:** A maxterm is the complement of a minterm. When writing a maxterm for a row where the output is 0, complement the variable if it is 1, and leave it uncomplemented if it is 0.
- **Assuming POS is always simpler:** Simplicity depends on the function. Always try both forms when optimizing.
- **Forgetting don't-cares:** Don't-care conditions can significantly reduce the POS expression if used correctly.

ADVANCED TOPICS: MULTI-LEVEL LOGIC AND POS

While POS is commonly taught as a two-level form (OR-AND), real circuits often use multi-level logic to reduce gate count or improve signal integrity. Decomposing a POS expression into smaller sub-expressions can lead to tree structures. For instance, a three-level NOR-NOR-NOR circuit might implement a large POS expression more efficiently. Additionally, the concept of **prime implicates** in POS is analogous to prime implicants in SOP. Algorithms like Quine-McCluskey can be adapted to find minimal POS by working on the zeros of the function.

PRACTICAL APPLICATIONS IN MODERN ELECTRONICS

Product of sums boolean algebra is not just theoretical; it appears in:

- **Arithmetic logic units (ALUs):** Many ALU control signals are implemented using POS due to regularity.
- **Memory address decoders:** NOR-based decoders are common in flash memories, leveraging POS forms.
- **Programmable logic arrays (PLAs):** PLAs can be programmed for either SOP or POS by appropriately configuring the AND and OR planes.
- **Circuit minimization algorithms:** Logic synthesis tools, such as Espresso, can output both SOP and POS minimized forms, and understanding them allows engineers to manually tweak results.

CONCLUSION

Product of sums boolean algebra is a fundamental technique for representing and simplifying logic expressions. By understanding how to derive POS from truth tables, K-maps, and algebraic manipulation, you gain the flexibility to choose the best representation for your design goals. Whether you need a compact NOR-only circuit or a low-latency decoder, the POS form offers a powerful alternative to the more common sum of products. As you continue working